

# Some initial thoughts on the decay-ring RF system

Erk Jensen

AB/RF

22-Oct-2008



# Setting the scene:

- Ring circumference:  $6911.6 \text{ m} = 23.05 \mu\text{s}$
- Harmonic numbers:
  - 40 MHz: 924
  - 80 MHz: 1848
- Bunch charge:  $10 \cdot 3.7\text{E}12 \text{ e} = 5.9 \mu\text{C}$  (!)
- Beam current:
  - 237 A during batch (20 bunches, 500 ns),
  - 5.1 A average (924 buckets, 23  $\mu\text{s}$ ).

Problems: very heavy and very transient beam loading!




**First, let's just look at a cavity from  
the beam (without any RF amplifier):**






## ... now imagine a cavity with (just) a 100 k $\Omega$ shunt impedance!

- For short bunches, the RF component of the beam current is  $I_B = 474$  A.  
(compare: LHC beam in PS: 2.1 A)
  - In 100 k $\Omega$ , this current would induce an RF voltage of 47 MV in steady state!
  - Of course, for a high  $Q$  cavity, this steady state would not be reached during 20 bunches, but the induced voltage would behave (solution periodic with 23  $\mu$ s) like:
- 
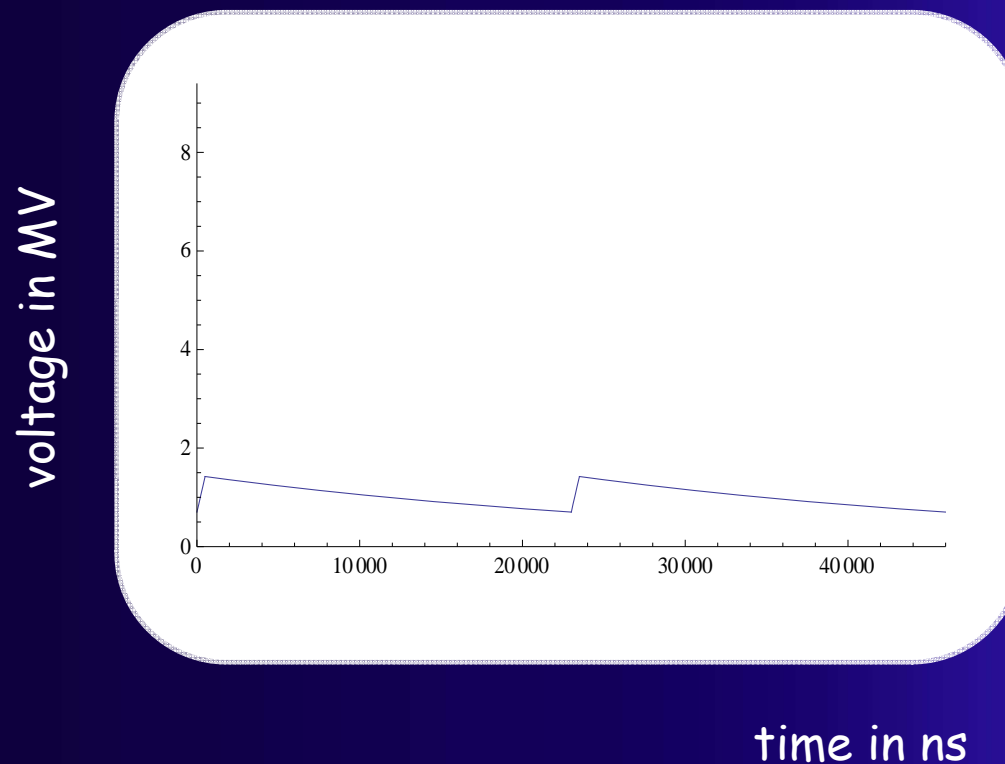
# Induced voltage

assuming  $R = 100 \text{ k}\Omega$  and  $Q = 4000$



It should not surprise that the average induced voltage is around 1 MV, i.e.  $100 \text{ k}\Omega \cdot 10.2 \text{ A}$



# But: what about the power?

- However, if these 100 k $\Omega$  were real, the power lost in to them would be

$$0.5 \cdot 10.2 \text{ A} \cdot 1.02 \text{ MV} = 5.2 \text{ MW}$$

... which of course would mean that the beam power would be lost rapidly!


(20 MJ are stored in the beam)

- ... and if it were a reactive impedance? Then the beam could induce by itself the voltage necessary! From the power balance this works, but it would make the beam (Robinson) unstable.



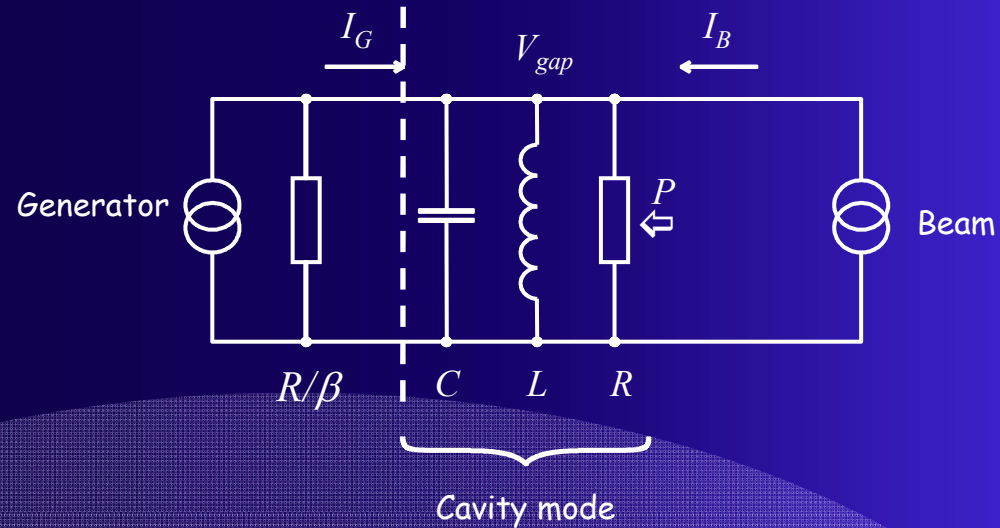**Now let's see cavity and beam  
from the amplifier:**






- The beam current shall be in quadrature to the gap voltage - it should be a "reactive", i.e. a "non-resistive" current.
- This means that there is no net power flow to or from the beam.
- Above transition, in the stable point of the stationary bucket this current is inductive.
- This current can be compensated by tuning the cavity down, e.g. by adding a parallel  $C$ .
- The relative detuning should be  $\frac{R I_B}{Q_{SCB}}$ .
- In this case, the generator would only have to deliver the power lost in the cavity (high  $Q$  preferable!)




Im

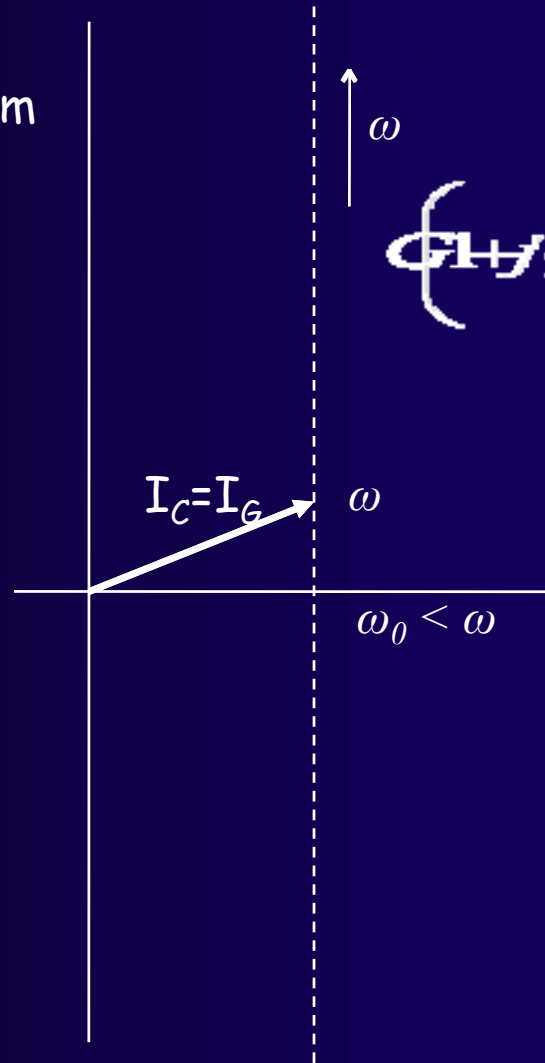

no beam, some mismatch

$$\left(1 + j \left( \frac{\omega - \omega_0}{Q} \right)\right)$$

Re (direction of  $V_{gap}$ )

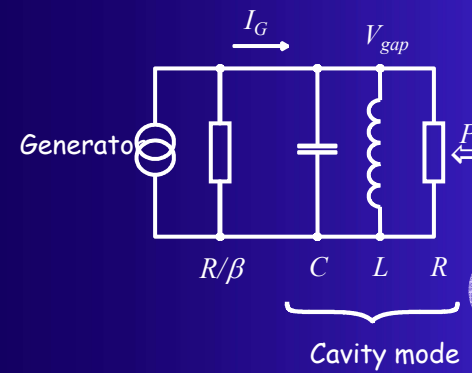

Im


no beam, tuned to match

$$\left(1 + j \left( \frac{\omega - \omega_0}{Q} \right)\right)$$

$$I_C = I_G$$

$$\omega_0 = \omega$$

Re


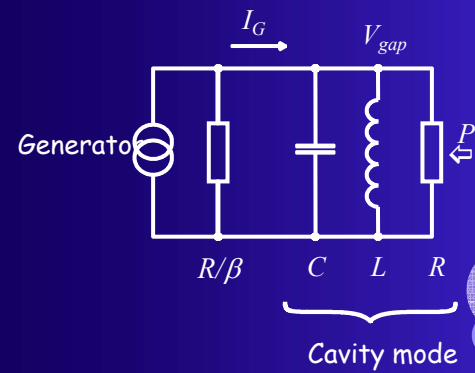






Im


beam on, matching lost
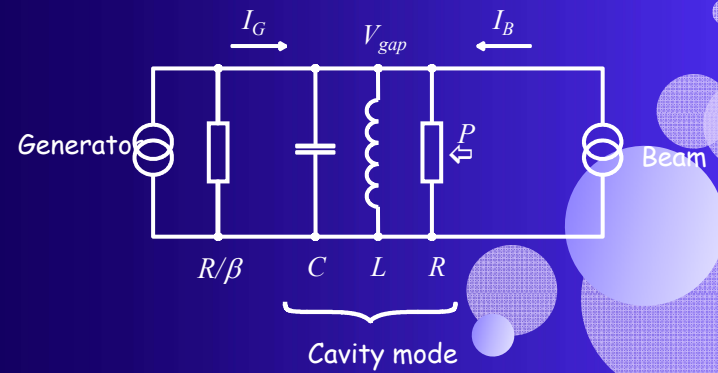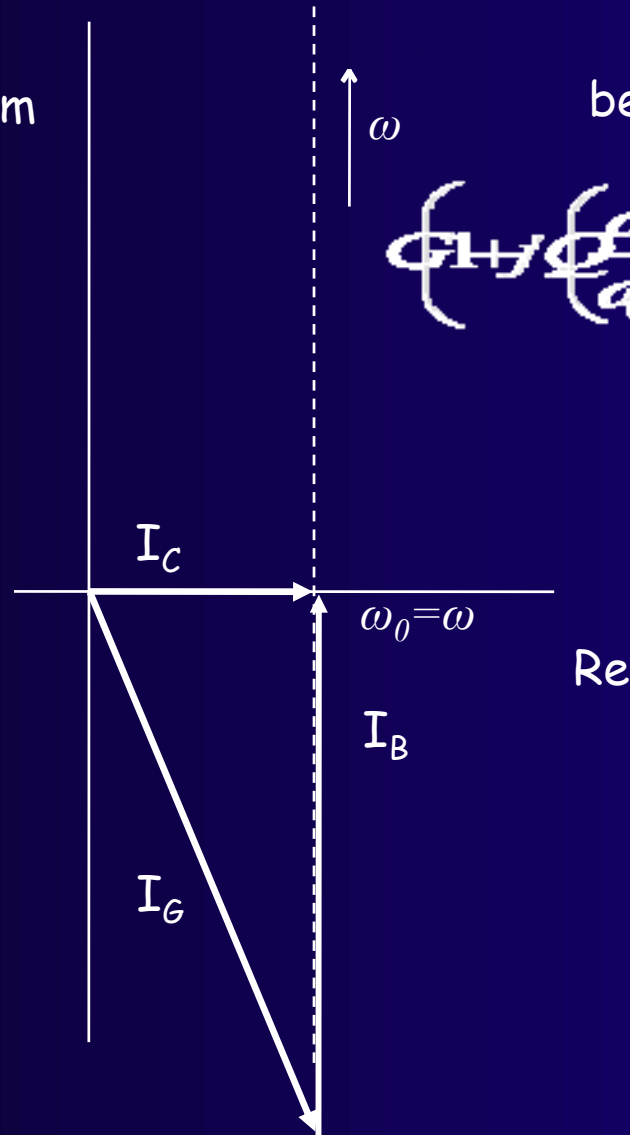
$$\left(1 + j \left( \frac{\omega - \omega_0}{Q} \right)\right)$$



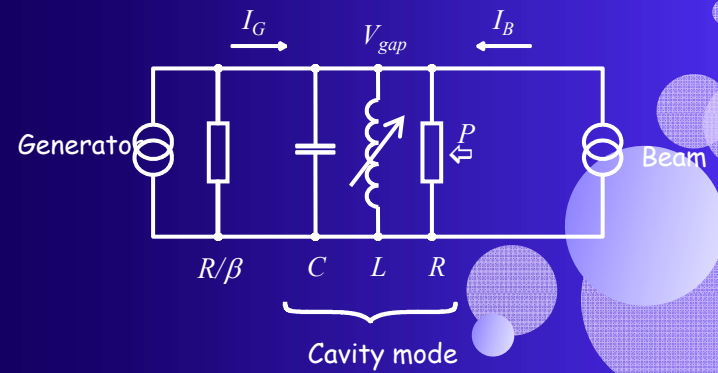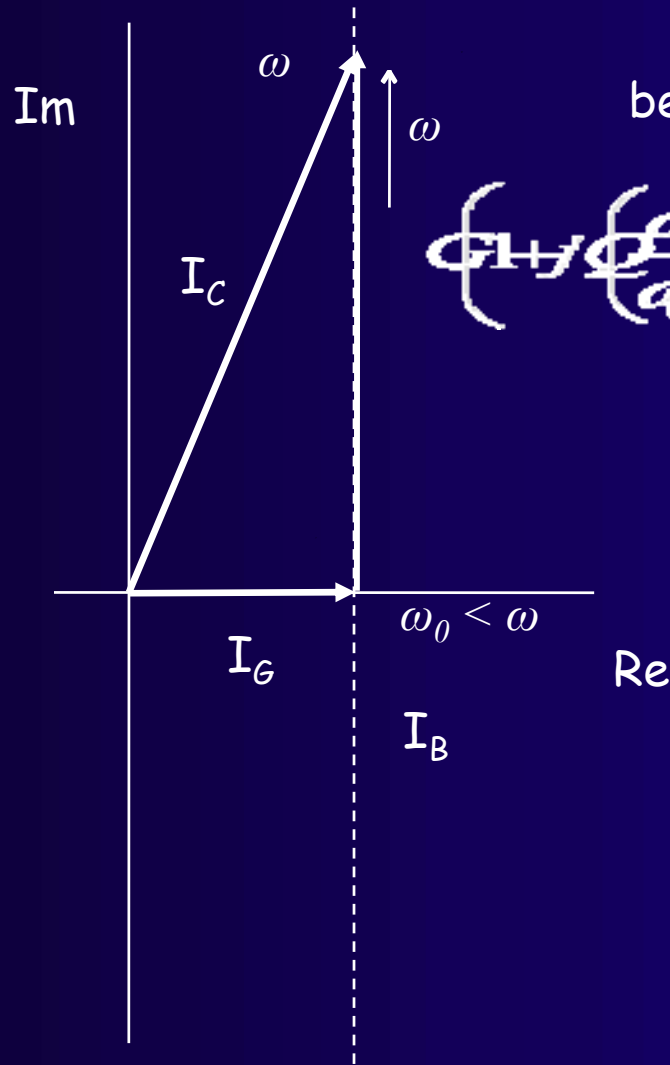





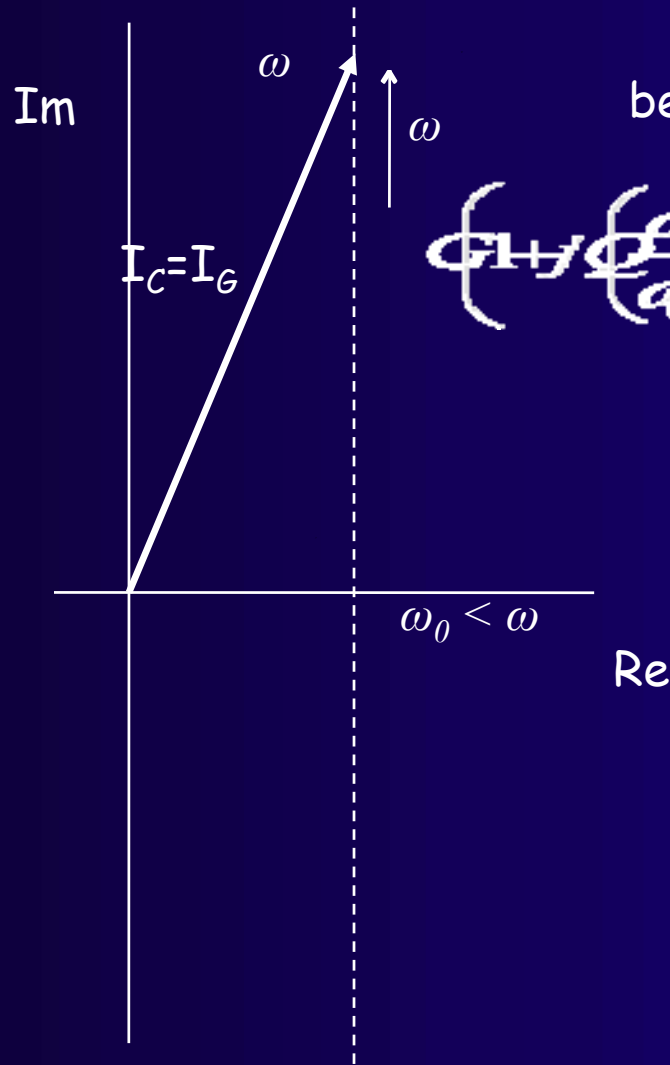

beam off, sudden mismatch
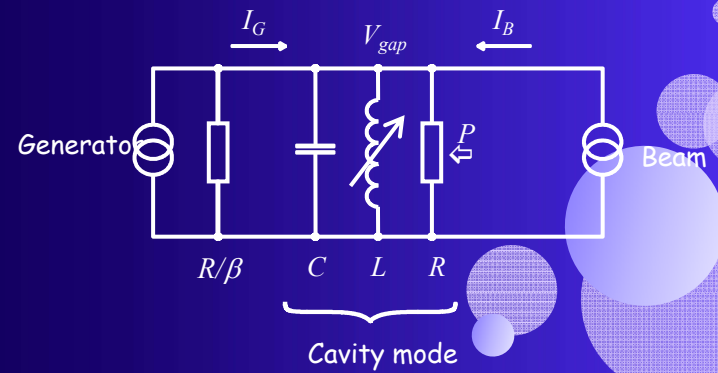
$$\left( \frac{1}{Y} \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right)$$



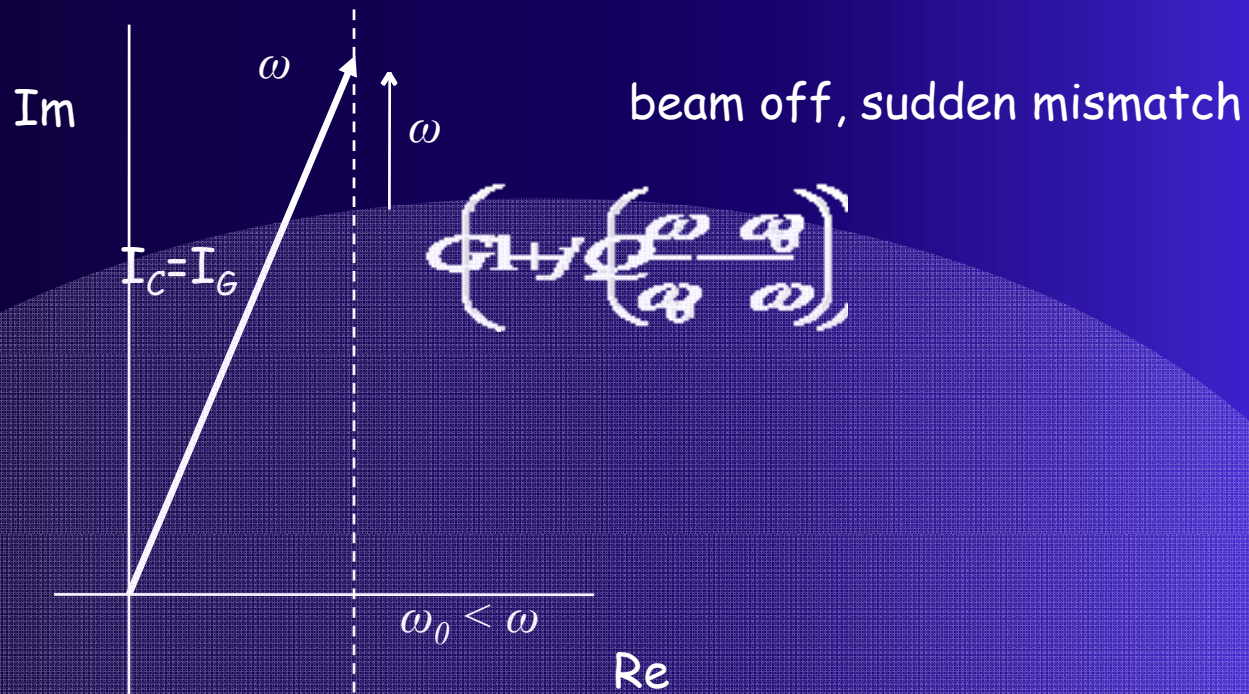


- In absence of the beam, one could allow an arbitrary gap voltage.
- For example, one could continue to feed power at  $\omega_0 < \omega$  where the cavity is tuned.
- But  $23 \mu\text{s}$  later, phase & amplitude must be correct again!



# For example:

- $Q: 20\,000, R: 500\text{ k}\Omega, V_{gap}: 300\text{ kV}, I_B: 474\text{ A}$
- $f: 40\text{ MHz} (h: 924)$ , beam on 20 periods (500 ns)
- result:  $f_0: 39.218\text{ MHz}$
- Integrated phase slip:  $(40-39.218) \cdot 0.025 \cdot 904$  turns = 17.67 turns; chose closest integer (18) ...
- ... so in absence of beam, feed  $f_{opt}: 39.203\text{ MHz}$ !
- The RF power amplifier has to deliver 90 kW in this example.

# Result of transient analysis:

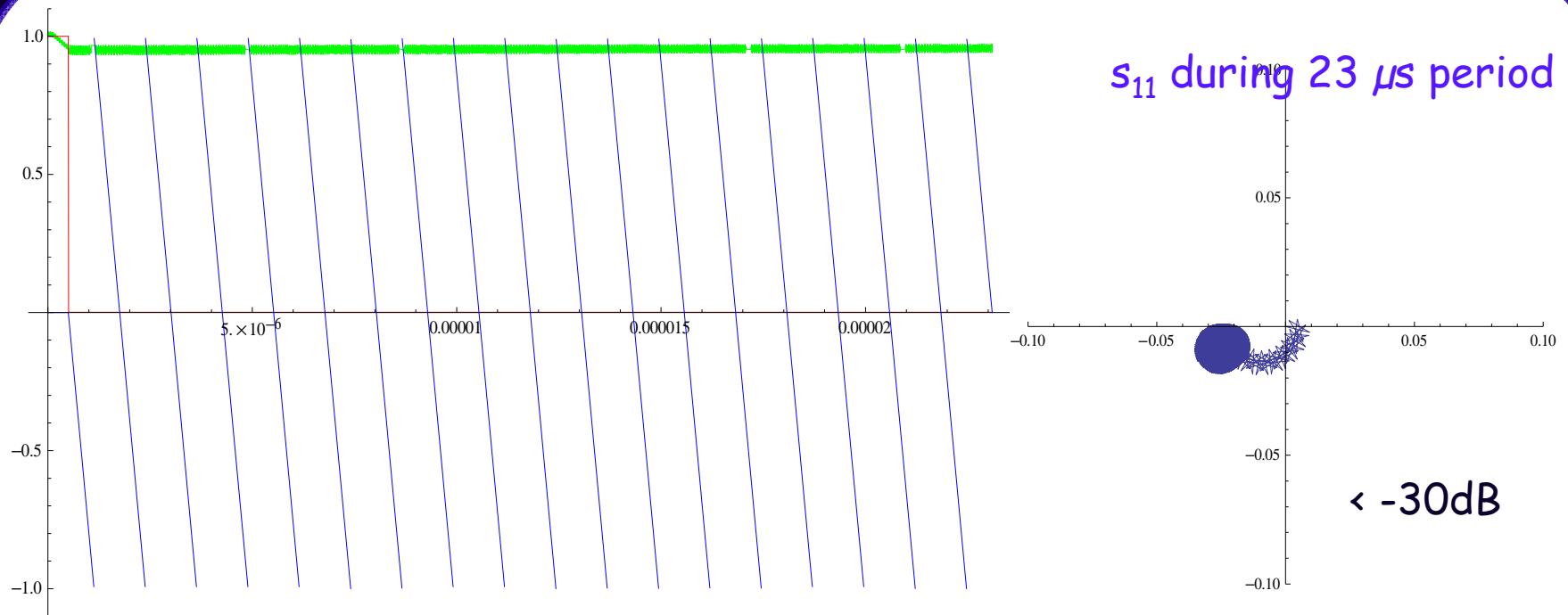

Blue: phase of drive current in units of  $\pi$  (corresponding to frequency offset)

Green: gap voltage in units of 300 kV

Red: total current in units of 474 A



# Summary:

- Not conclusive yet - only first ideas - more work is needed!
- The heavy transient beam loading is unprecedented.
- Since there is no net energy transfer to the beam, the problem might be solved using a linear phase modulation in the absence of the beam, mimicking detuning - this could reduce gap transients.
- A high Q cavity (S.C.?) would be preferable.